

**CS2100 Assignment #2**  
 AY2024/25 Semester 1  
**Deadline: Monday, 14 October 2024, 1:00pm**  
 TEMPLATE FOR SUBMISSION

Full name: Yang Hanming

Tutorial grp: T 10

**Q1. (Total: 15 marks)**

Cycle time: 13 ps [4 marks]

Clock frequency: 76.923 GHz [3 marks]

Time taken for beq instruction: 6 ps [3 marks]


Optimization: new ALU [5 marks]

Explain your answers below.

lw → Reg file + ALU + Mem read + reg file  
 sw → Reg file + ALU + Mem write  
 beq → Reg file + ALU  
 addi → Reg file + ALU + Reg file

<p>Optimize ALU</p> $lw = 2 + 2 + 5 + 2$ $= 11ps$ $sw = 2 + 2 + 7$ $= 11ps$ $beq = 2 + 2$ $= 4ps$ $addi = 2 + 2 + 2$ $= 6ps$	<p>Optimize Reg file</p> $lw = 1 + 4 + 5 + 1$ $= 11ps$ $sw = 1 + 4 + 7$ $= 12ps$ $beq = 1 + 4$ $= 5ps$ $addi = 1 + 4 + 1$ $= 6ps$	<p>Optimizing ALU will        result in faster sw and        beq instructions, and equal        time for lw and addi</p>
--	---	--

**Q2. (Total: 5 marks)**

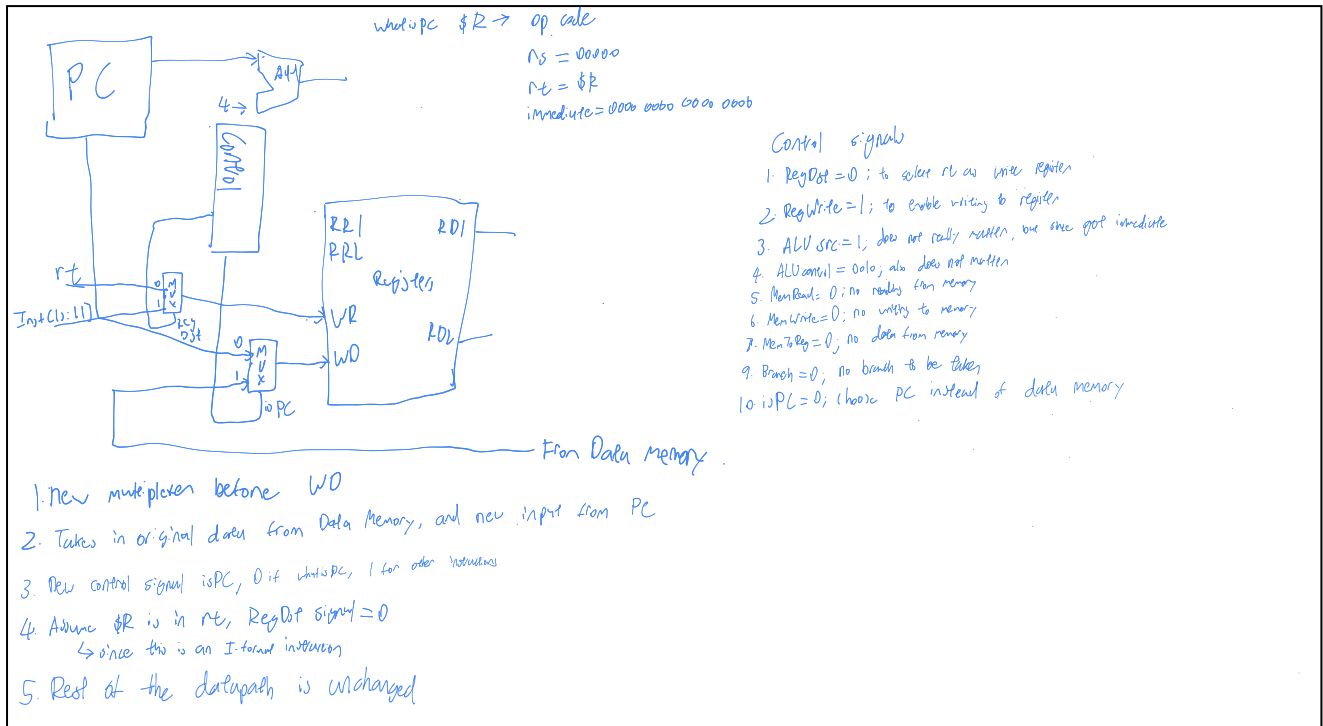

**Q3. (Total: 3 marks)**

(a)  $M_{31} = A + B' + C' + D' + E' + F'$  [1 mark]

(b)  $m_{29} \cdot M_{31} =$   $A' \cdot B \cdot C \cdot D \cdot E' \cdot F$  [2 marks]


**Q4. (Total: 4 marks)**

(a)  $F \cdot G' = \sum m(\quad 7, 13, 15 \quad)$  [2 marks]

(b)  $G' \oplus H = \Sigma^m(1, 5, 8, 12)$  [2 marks]

**Q5. (Total: 3 marks)**

Draw your circuit below.

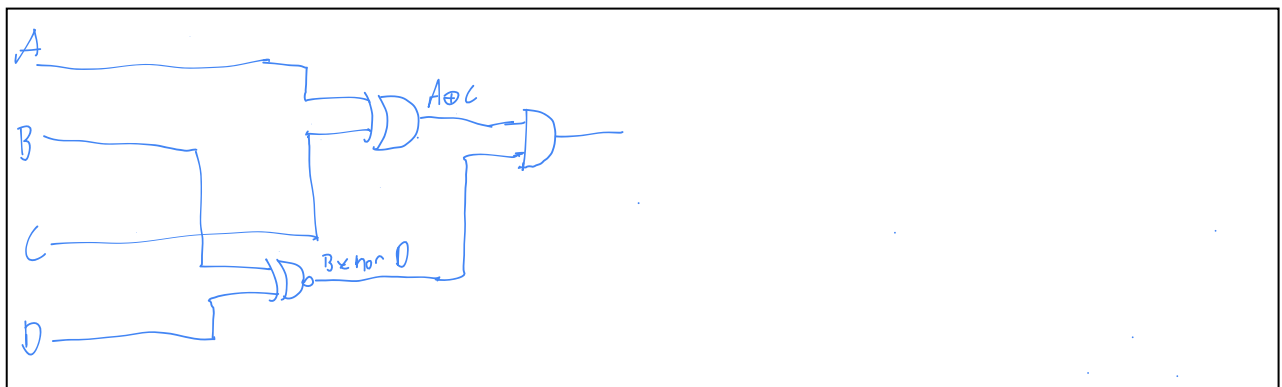

**Q6.** (Total: 7 marks)

(a) Number of PIs in the K-map of Z:

6

[1 mark]

(b) Number of EPIs in the K-map of Z:

1

[1 mark]

(c) Number of distinct simplified SOP expressions for Z:

3

[1 mark]

(d) One simplified SOP expression for Z:

[2 marks]

$$B \cdot C + B' \cdot D + A' \cdot B'$$

(e) One simplified POS expression for Z:

[2 marks]

$$(B' + C) \cdot (A' + B + D)$$

**Q7.** (Total: 3 marks)

(a)

[1 mark]

A	B	C	D	IsZero
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

(b) Simplified SOP expression

[2 marks]

$$IsZero = A' \cdot B' \cdot C' \cdot D' + A' \cdot B \cdot C' \cdot D + A \cdot B' \cdot C \cdot D' + A \cdot B \cdot C \cdot D$$

## Workings

Write your workings here. They will not be graded, but the grader might look at it to figure out where you went wrong.

## Workings for Q3

$$M31 = 011 \quad 111$$

$$M31 = A + B' + C' + D' + E' + F'$$

$$m29 = 011 \quad 101$$

$$= A' \cdot B \cdot C \cdot D \cdot E' \cdot F$$


$$m29 \cdot M31 = (A + B' + C' + D' + E' + F') \cdot (A' \cdot B \cdot C \cdot D \cdot E' \cdot F)$$

$$= ((A + B' + C' + D' + E' + F') \cdot A') \cdot (B \cdot C \cdot D \cdot E' \cdot F), \text{ by commutative law}$$

$$= (A' \cdot B' + A' \cdot C' + A' \cdot D' + A' \cdot E' + A' \cdot F') \cdot (B \cdot C \cdot D \cdot E' \cdot F), \text{ by distributive and identity law}$$

$$= A' \cdot B \cdot C \cdot E' \cdot F$$

## K-map for Q6

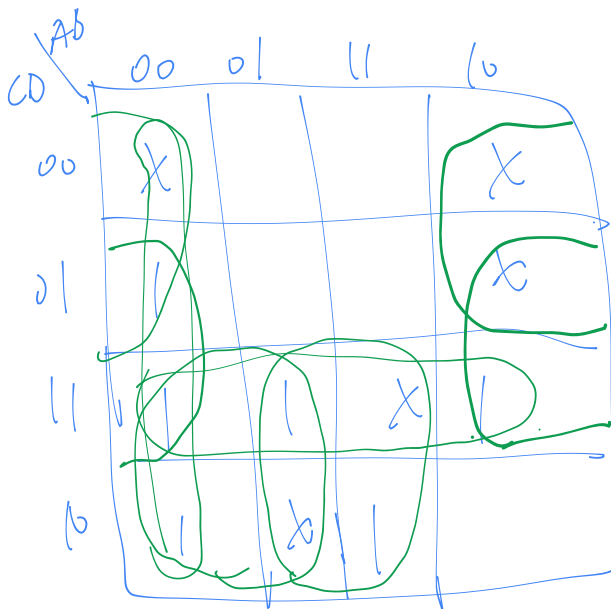

$$PI = 6$$

$$EPI = 1$$